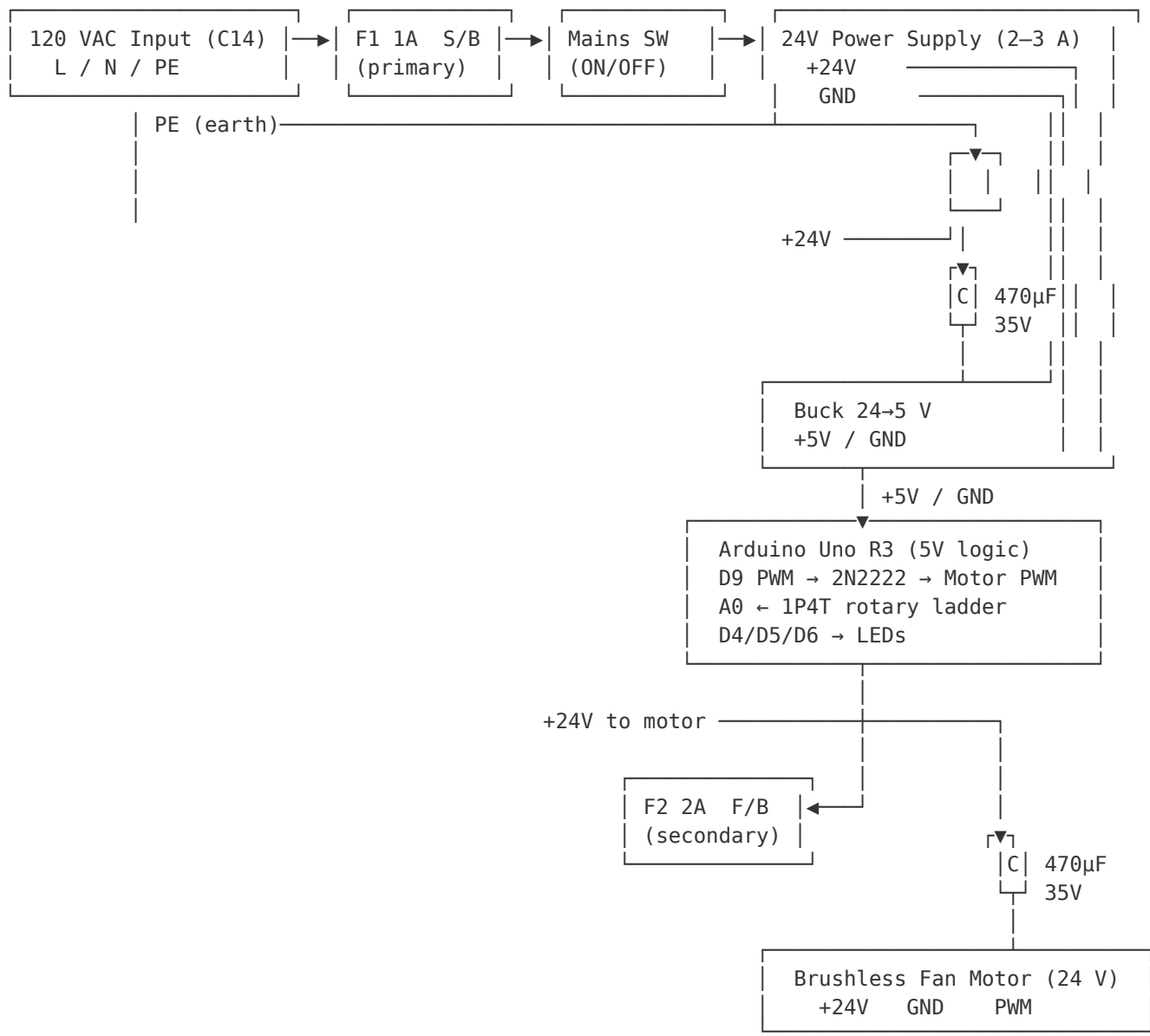



# Arduino Uno 24 V Brushless Fan Controller – Block Wiring (with F1/F2 and bulk caps)



Rotary ladder (A0 input):  
+5V – 10k – nodeH – 10k – nodeM – 10k – nodeL – 10k – GND  
OFF → GND, LOW → nodeL (~1.25 V), MED → nodeM (~2.5 V), HIGH → nodeH (~3.75 V)  
A0 = rotary common; add 0.1 µF from A0 → GND near Uno.

Legend: F1 = primary fuse (slow-blow), F2 = 24 V motor fuse (fast-blow), = earth bond, C = bulk capacitor.
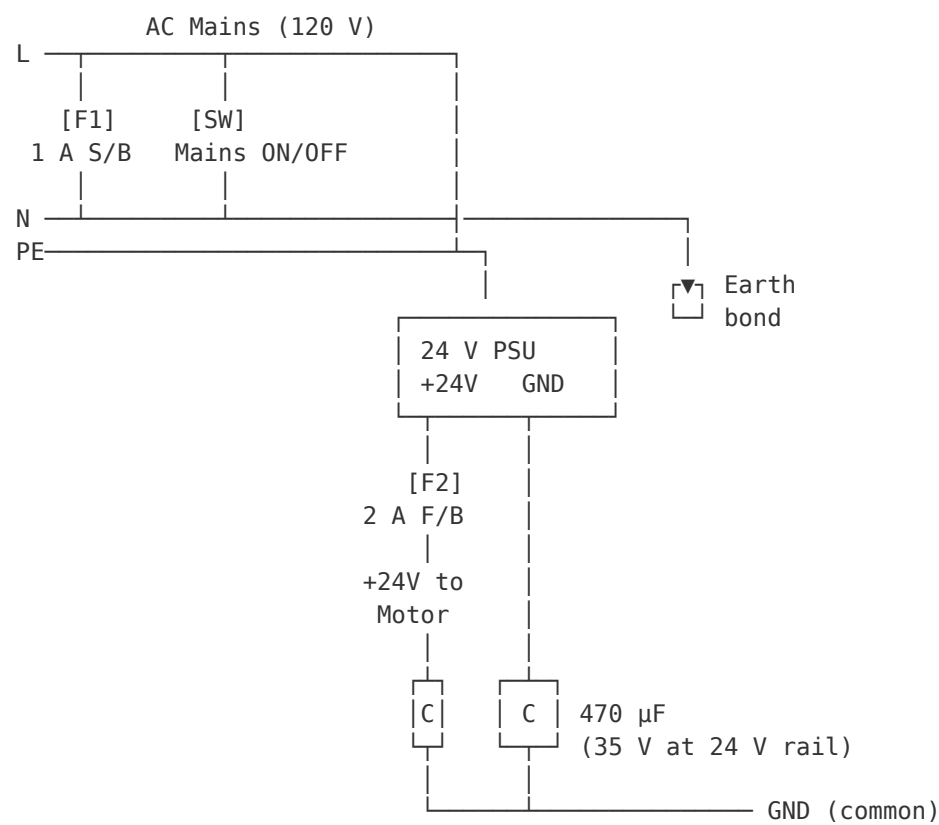
# Arduino Uno 24 V Brushless Fan Controller – Symbolic Schematic (with F1/F2 and bulk caps)



Buck 24→5 V:

+24 V → IN+

GND → IN-

OUT+ (5 V) → Arduino 5V

OUT- (GND) → Arduino GND

Arduino + PWM driver:

D9 → 1 kΩ → base 2N2222 emitter — GND

+5 V → 10 kΩ → (pull-up)

PWM line to motor  
(optional 100 Ω series, 1 nF to GND)

LEDs: D4/D5/D6 → 330 Ω → GND

Rotary: A0 reads 1P4T ladder (+5 V–10k–nodeH–10k–nodeM–10k–nodeL–10k–GND; OFF→GND; LOW/MED/HIGH→nodes)

Note: Add 470 µF / 10 V across Arduino 5 V and GND near the board (bulk decoupling).

# Arduino Uno 24 V Brushless Fan Controller – Breadboard / Prototyping (with F1/F2 and bulk caps)

Breadboard / prototype checklist (with fuses and bulk caps):

Primary (AC side):

- IEC C14 → [F1 1 A slow-blow] → Mains Switch → 24 V PSU (L line)
- N line goes directly to PSU N. PE (earth) bonded to chassis ( ).

24 V side (DC):

- PSU +24 V → [F2 2 A fast-blow] → Motor +24 V terminal
- PSU GND → Motor GND and system GND
- Bulk cap 470  $\mu$ F / 35 V across +24 V and GND near motor/controller
- Optional TVS 33 V across +24 V/GND

5 V logic:

- Buck IN: +24 V / GND from PSU
- Buck OUT: +5 V / GND to Arduino 5V/GND
- Bulk cap 470  $\mu$ F / 10 V across 5 V/GND near Arduino

PWM stage:

- D9 → 1 k $\Omega$  → 2N2222 base; emitter → GND; collector → Motor PWM
- 10 k $\Omega$  pull-up from Motor PWM → +5 V
- Optional: 100  $\Omega$  in series to Motor PWM, 1 nF C0G to GND at motor end

Rotary ladder (A0):

- +5 V – 10k – nodeH – 10k – nodeM – 10k – nodeL – 10k – GND
- Rotary OFF→GND, LOW→nodeL, MED→nodeM, HIGH→nodeH; common → A0
- 0.1  $\mu$ F from A0 → GND near Arduino

LEDs:

- D4/D5/D6 → 330  $\Omega$  → LEDs → GND

Grounding & layout:

- Keep AC and low-voltage wiring separated; observe creepage/clearance.
- Twist PWM with GND if cable > 30 cm.
- Earth-bond any metal enclosure.